

# BLG222E - Computer Organization

## Assignment I

Design a 4 – *bit* register (shown in the figure) that has 2 4 – *bit* input (A and B), 1 – *bit* control input (s) and 4 – *bit* output. This register should compare A and B **as unsigned integers** and if  $s = 0$ , then  $Q^+ = \min(A, B)$  and if  $s = 1$ , then  $Q^+ = \max(A, B)$ . For example, if the inputs of this register are  $A = 0111$  and  $B = 1000$ :  $Q^+ = 0111$  if  $s = 0$  and  $Q^+ = 1000$  if  $s = 1$ .

You should use D flip-flops, adder, multiplexer, logic gates etc. in your design. Implement your design in Logisim software, save your design in *.circ* format, and upload it to Ninova before its deadline.

